



**FACULTY OF ENGINEERING**  
**END OF SEMESTER EXAMINATIONS - APRIL 2025**

**PROGRAMME: DIPLOMA IN ELECTRICAL AND CONTROL ENGINEERING**

**YEAR/SEM: YEAR 1/SEMESTER 2**

**COURSE CODE: DEE1202**

**NAME: ELECTRICAL ENGINEERING SCIENCE II**

**DATE: 2025-04-14**

**TIME: 2:00-5:00PM**

**INSTRUCTIONS TO CANDIDATES:**

1. Read the instructions very carefully
2. The time allowed for this examination is STRICTLY three hours
3. Read each question carefully before you attempt and allocate your time equally between all the Sections
4. Write clearly and legibly. Illegible handwriting cannot be marked
5. Number the questions you have attempted
6. Use of appropriate workplace examples to illustrate your answers will earn you bonus marks
7. Any examination malpractice detected will lead to automatic disqualification.

**DO NOT WRITE ANYTHING ON THE QUESTION PAPER**

## Section A Attempt any 2 questions in Section A

### Question 1:

A circuit consists of a  $10\mu\text{F}$  capacitor connected in series with a  $25\text{k}\Omega$  resistor with a switchable  $100\text{V d.c.}$  supply. When the supply is connected,

Calculate

- The time constant (03 marks)
- The maximum current (03 marks)
- The voltage across the capacitor after  $0.5\text{s}$  (04 marks)
- The current flowing after one time constant (04 marks)
- The voltage across the resistor after  $0.1\text{s}$  (05 marks)
- The time for the capacitor voltage to reach  $45\text{V}$  (06 marks)

### Question 2:

- Explain briefly what happens when a capacitor is connected in series with a resistor across a DC supply source. Write relevant equations to support your answer (09 marks)
- A capacitor is charged to  $100\text{V}$  and then discharged through a  $50\text{k}\Omega$  resistor. If the time constant of the circuit is  $0.8\text{s}$ , determine:
  - The value of the capacitor (04 marks)
  - The time for the capacitor voltage to fall to  $20\text{V}$  (04 marks)
  - The current flowing when the capacitor has been discharging for  $0.5\text{s}$  (04 marks)
  - The voltage drop across the resistor when the capacitor has been discharging for one second. (04 marks)

### Question 3:

- An alternating current completes 5 cycles in  $8\text{ms}$ . What is its frequency? (04 marks)
- An alternating voltage  $v$  has a periodic time of  $20\text{ms}$  and a maximum value of  $200\text{V}$ . When time  $t=0$ ,  $v=-75\text{volts}$ . Deduce a sinusoidal expression for  $v$  and sketch one cycle of the voltage showing important points. (05 marks)
- Plot a sine wave of peak value  $10.0\text{A}$ . Show that the average value of the wave form is  $6.37\text{A}$  over half a cycle, and that the r.m.s. value is  $7.07\text{A}$  (10 marks)
- Determine the peak and mean values for a  $240\text{V}$  mains supply. (05 marks)


### Question 4:

- a. Explain briefly what happens when a capacitor is connected in series with a resistor across a DC supply source. Write relevant equations to support your answer (09 marks)
- b. A coil of inductance  $0.04\text{H}$  and resistance  $10\Omega$  is connected to a  $120\text{V d.c.}$  supply. Determine
  - i. The final value of current,
  - ii. The time constant of the circuit
  - iii. The value of current after a time equal to the time constant from the instant the supply voltage is connected

## Section B Attempt any 2 questions in Section B

### Question 1:

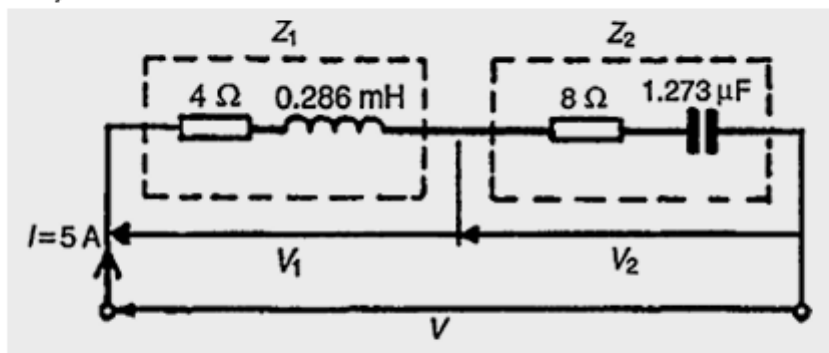- a. Define the term Resonance in an R-L-C circuit (02 marks)
- b. Determine the p.d.s  $V_1$  and  $V_2$  for the circuit shown in Figure if the frequency of the supply is  $5\text{ kHz}$ , determine the supply voltage  $V$  and the circuit phase angle. (13 marks)



- b. The current at resonance in a series L-C-R circuit is  $100\mu\text{A}$ . If the applied voltage is  $2\text{mV}$  at a frequency of  $200\text{ kHz}$ , and the circuit inductance is  $50\mu\text{H}$ , find
  - i. The circuit resistance (05 marks)
  - ii. The circuit capacitance. (05 marks)

### Question 2:

- a. Explain briefly what happens when a capacitor is connected in series with a resistor across a DC supply source. Write relevant equations to support your answer (09 marks)
- b. A coil of inductance  $0.04\text{H}$  and resistance  $10\Omega$  is connected to a  $120\text{V}$  d.c. supply. Determine
  - i. The final value of current,
  - ii. The time constant of the circuit
  - iii. The value of current after a time equal to the time constant from the instant the supply voltage is connected

**Question 3:**

A coil consists of a resistance of  $100\Omega$  and an inductance of  $200\text{ mH}$ . If an alternating voltage,  $v$ , given by  $v=200\sin 500t$  volts is applied across the coil, Calculate

- (a) The circuit impedance, (5 marks)
- (b) The current flowing, (5 marks)
- (c) The p.d. across the resistance, (5 marks)
- (d) The p.d. across the inductance (5 marks)
- (e) The phase angle between voltage and current. (5 marks)

**Question 4:**

- a. A transformer has a rated output of  $200\text{kVA}$  at a power factor of  $0.8$ . Determine the rated power output and the corresponding reactive power. (05 marks)
- b. A circuit consisting of a resistor in series with a capacitor takes  $100\text{ watts}$  at a power factor of  $0.5$  from a  $100\text{V}$ ,  $60\text{Hz}$  supply. Find
  - i. The current flowing (05 marks)
  - ii. The phase angle (05 marks)
  - iii. The resistance, the impedance (05 marks)
  - iv. The capacitance. (05 marks)